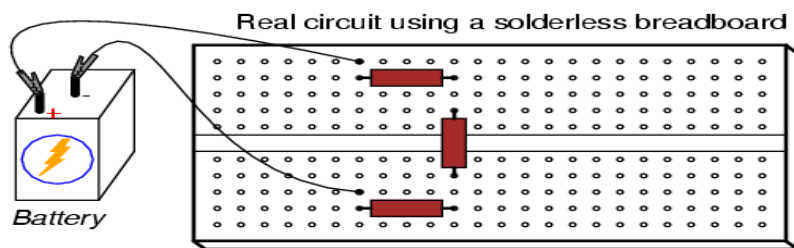


End of Term Exam Detail		Trainee's Detail	
SECTOR:	ICT	Trainee's Name:
TRADE:	NETWORKING	Trainer's Name:	NIZEYIMANA Eraste
ModuleCode		Module Title	GENERAL ELECTRONICS
LEVEL:	3	Date:/..... 2023

1. Draw schematic diagram of the following circuit



1. With examples , explain the group of Electronics components
2. What is the color code of 333k ohms +- 5% five band resistor?
3. Write all color code of 4 BAND COLOR CODE Resistor
4. List 5 use of DIGITAL MULTIMETER
5. Copy and complete
 - A. A printed circuit board is used to
 - b. Resistance is the property of a component which restricts the flow of electric current. It is measurable quantity and it

Good Luck!!!!